# WOMEN'S UNIVERSITY IN AFRICA



Addressing gender disparity and fostering equity in University Education

## FACULTY OF MANAGEMENT AND ENTREPRENEURIAL SCIENCES

## BSc HONOURS DEGREE IN COMPUTER SCIENCE

#### **MAIN PAPER**

HCS 113: LOGIC DESIGN & SWITCHING CIRCUITS

INTAKE 3: FIRST YEAR FIRST SEMESTER

**TIME: 2 HOURS AFTERNOON** 

## INSTRUCTIONS TO CANDIDATES

Answer any four questions.

#### **QUESTION 1**

Design an 8 bit register.


[25]

#### **QUESTION 2**

Using Boolean algebra rules, do the following

a) Simplify the following logic expression

[10]

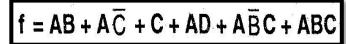

b) List out the Basic Theorems and Properties of Boolean Algebra. Justify with Proof. [15]

#### **QUESTION 3**

- a) Write brief notes on the following
  - i. SIPO;
  - ii. PIPO;
  - iii. SISO; and
  - iv. PISO.

[8]

b) Draw and explain the block diagram of PLA.

[9]

- c) Design the following
  - i. Half adder; and
  - ii. Full adder

[8]

## **QUESTION 4**

a) Differentiate between encoder and decoder

[6]

b) Differentiate between multiplexer and decoder

- [6]
- c) Differentiate between Asynchronous Counters and synchronous counters
- r*a*n

d) Draw the J-K flip flop and truth table

[7]


[6]

# **QUESTION 5**

a) What does and EXOR gate do

[6] [6]

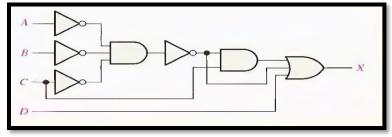b) Reduce (Simplify) the logic circuit in to a minimum form.



c) Express the Boolean function

$$D = (\overline{A} + B)(\overline{B} + C)$$

i. As a product of maxterms. [7]ii. As a sum of minterms. [6]

# **QUESTION 6**

- a) Convert the hexadecimal number 4B3 to decimal notation. What about the decimal equivalent of the hexadecimal number 4B3.3? [4]
- b) Convert 234.14 expressed in an octal notation to decimal. [4]
- c) Consider converting 101102 to base 8 [3]
- d) Convert number 11001111 to hexadecimal [3]
- e) Use a **K-map** to simplify the Boolean expression

$$E = \overline{A}\overline{B}\overline{C}D + \overline{A}CD + \overline{A}\overline{C} + C$$

[5]

f) Design the function  $(A, B, C, D) = \sum m (1, 4, 5, 8, 10, 12, 13)$  using 8x1 multiplexer. [6]

**END**